

Latch (Level-Sensitive) Timing Diagrams

 


Figure 1: RS Latch

The Q (and \bar{Q}) output will change if either of the \bar{R} or \bar{S} input signals change.

 


Figure 2: RS Latch w/Enable

The Q (and \bar{Q}) output will change if either of the R or S input signals change when the E input signal is high (or becomes high.)

 


Figure 3: D Latch

The Q output will change to match the D input signal any time that the E input signal is high.

Flip-Flop (Edge-Sensitive) Timing Diagrams

 


Figure 4: D Flip-Flop (falling-edge triggered)

The Q signal will be set to match that of the D signal when ever a falling edge on clk occurs.

(The *only* time that the Q output can change as a result of a falling edge on the clk signal line.)