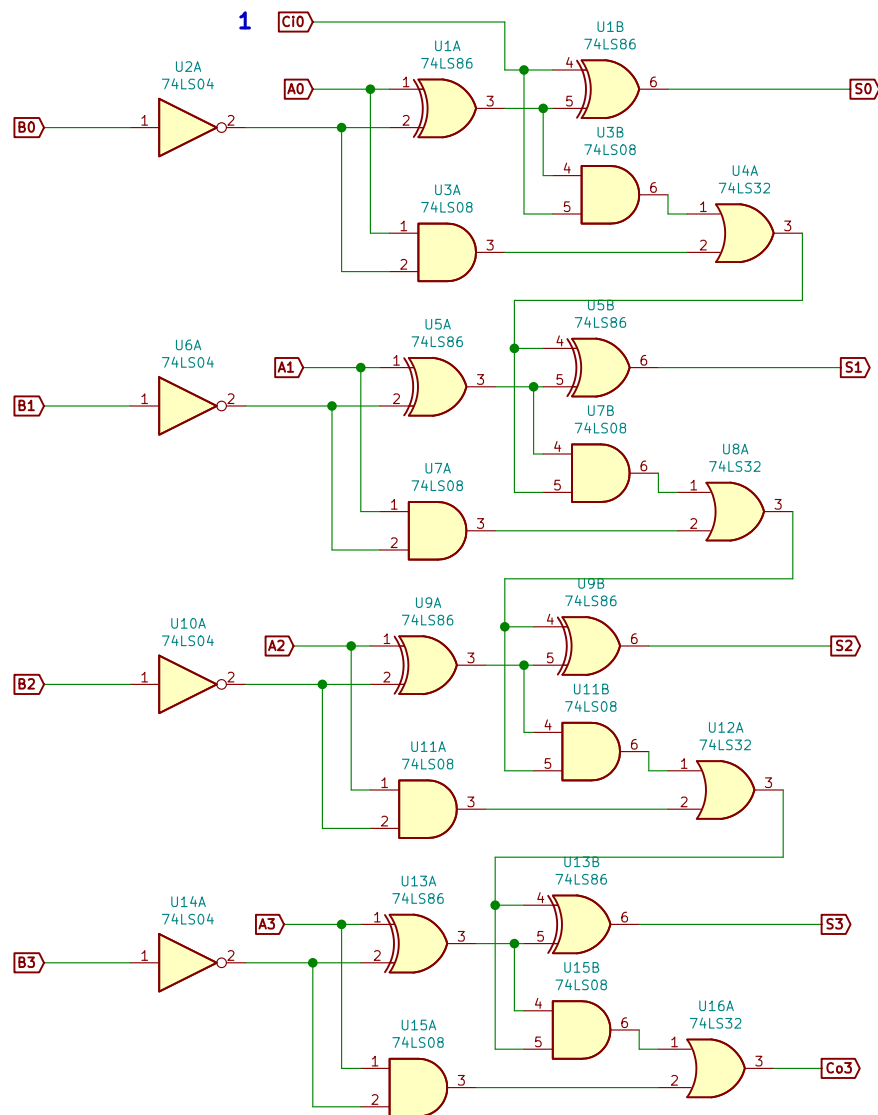


How Do We Subtract? Negate One Operand & Then Add them!



Copyright (C) 2019 John Winans

This documentation describes Open Hardware and is licensed under the CERN OHL v. 1.2.

You may redistribute and modify this documentation under the terms of the CERN OHL v.1.2. (<http://ohwr.org/cernohl>). This documentation is distributed WITHOUT ANY EXPRESS OR IMPLIED WARRANTY, INCLUDING OF MERCHANTABILITY, SATISFACTORY QUALITY AND FITNESS FOR A PARTICULAR PURPOSE. Please see the CERN OHL v.1.2 for applicable conditions

If you chose to manufacture products based on this design, please notify me (see license section 4.2) via jwinans@niu.edu

Sheet: /

File: 10-multibit-subtractor.sch

Title: 4-bit Subtractor

Size: USLetter Date: 2019-09-09

KiCad E.D.A. eeschema 5.1.5+dfsg1-2build2

Rev: 1

Id: 1/1